

Endre Balogh / VA6BGE

Interference and Noise troubleshooting

Presentation to SASTAR Group on April 19, 2021

Agenda

- 1. Current general station set-up
 - Interference during transmit
 - Noise mitigation Small example

- 5 HF antennas and dummy load on the roof,
 - Switching by IP based device located on the tower powered via Power over Ethernet only 2
 HF coax cables come down from the roof,
 - 1 vertical VHF/UHF antenna,
 - The shack is in the basement,
 - 1 HF radio, 1 handheld VHF/UHF radiom, 1 Amplifier, 1 Manual antenna tuner,
 - All coax cables come down to the basement through an unused gas furnace vent along with other wires (240V wires to solar panel inverters, Cat6 cables, rotator cable, etc.),
 - Station room is fed via 15AMP breaker (shared between many devices within the same room),
 - The low voltage devices are fed by a single 35AMP ferrite core transformer,
 - Amplifier has its own 2 x 20AMP circuit.












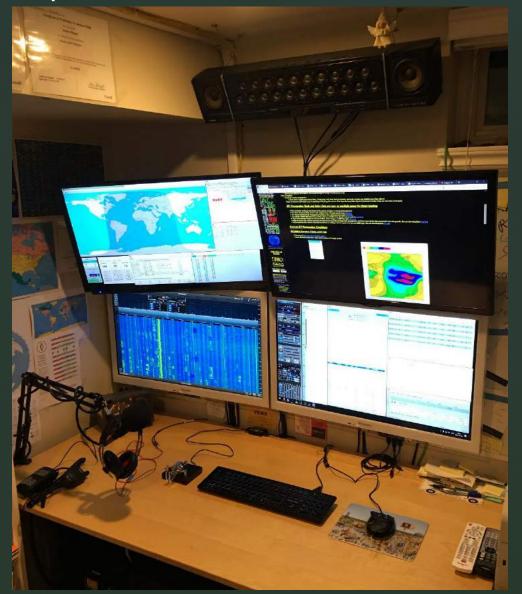

Interference during transmit – Power <100Watt

- Radio (IP based) kept on loosing connection with computer during transmit even as low as 40Watts
 - Same bands were not possible to use depending on the angle of the Hexbeam on the roof,
 e.g. 15m to Europe was not possible the radiation elements were dead above the antenna switch box on the tower,
- Loosing internet connection in the house while transmitting connection returned after 10-15sec from end of transmit – typically on 20 and 15m bands even at 80 to 100Watts,
- Interference in the house with sound systems typically on 40m even at 80Watts,
- USB tabletop speaker reliably crashed during 80m transmits at 80 Watts,
- Interference with dishwasher only on 160m already at 80Watts,
- Rotator USB controller failed on pretty much anytime transmitting above 80Watts,
- Rotation needle slightly moved during transmitting above 80Watts,

Interference during transmit – Power >100Watts

- Failing computer keyboard and mouse at around 150 to 250Watts on 40 and 20m bands,
 - Antenna switch (IP based) disconnect and directing power into dummy load typically around 200 – 400Watts on any band randomly,
 - Computer display shutdown (only 1 of the 4) typically on 80m only around 300Watts transmit power,
 - Computer shutdown at around 200-300Watts on 20m and around 400Watts on 40m,
 - Problems with some bathroom appliances using touch technology,
 - Not sure how the neighbors were impacted...

 Installed Chokes on each antenna feedline as close as it was possible to the radiating element – The small coax beads were useless














Installed ferrite rings onto low voltage cables – Got flat Ethernet cables



Installed ferrite rings onto wires going into computer




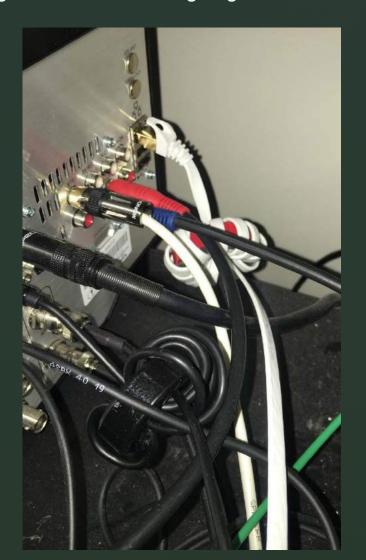Installed ferrite rings onto some wires going into the radio including the power cable



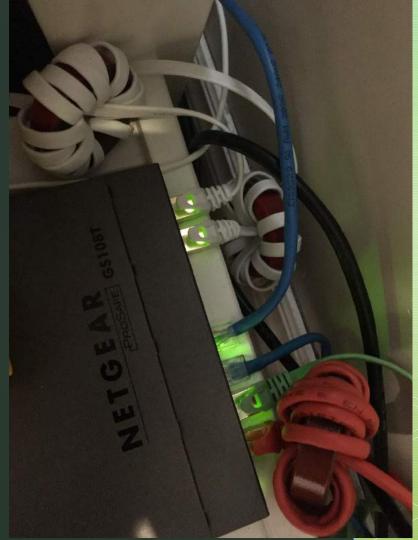Installed ferrite rings onto Ethernet cables and the switch in the room





• Installed ferrite rings onto the rotator control cable – the cable was too short to put on more



• Installed copper tape shield inside the antenna switch also on the PoE separator



• Got a second hand UPS for the Station - also good for noise filtering and back-up in case the

fuse blows



Interference during transmit – Results of the action

- No more interference on the home network during transmit,
 - The rotator and its controller does not indicate false directions during transmit (now it is only +/-5degrees instead of shutting down),
 - No more computer shutdown due to interference,
 - Significantly reduced noise on the sound amplifiers in the house,

 MORE CONFIDENT IN OPERATING knowing that the system is more reliable

Interference during transmit – Results of the action

• The dishwasher is still not happy (older Electrolux model with touch panel)

Breaker is shutdown prior to high power transmit → The plan is to place ferrite rings on its feedline



Interference during transmit – If I could re-build


- Use good quality shielded low voltage wires
 - CAT6 STP or better,
 - Good quality wires into the stereos (on the input side at least),
 - Leave extra length at both ends of the cables it is useful for installing ferrite rings or for splicing if the plug needs to be replaced,
 - Don't save on chokes the beads may not be sufficient,
 - Run wires on the shortest possible route to the shacks and try not to put them next to other wires –
 a separate conduit is a good idea,
 - Have a separate breaker for the radio itself,
 - Properly tuned antenna shall cause less RFI trouble particularly on high power.

Noise mitigation – The problem

- Experienced serious interference slightly on 40m (1 S unit), but significantly on 80 and on 160m when the fairy lights were on outside the house (up to 3 S units)
 - Approx. 1,000ft of fairy lights all over the shrubs
 - They work like a large radiating antenna
 - Fed by 8AMP 12Volt cheap switching power supply



Noise mitigation – The problem

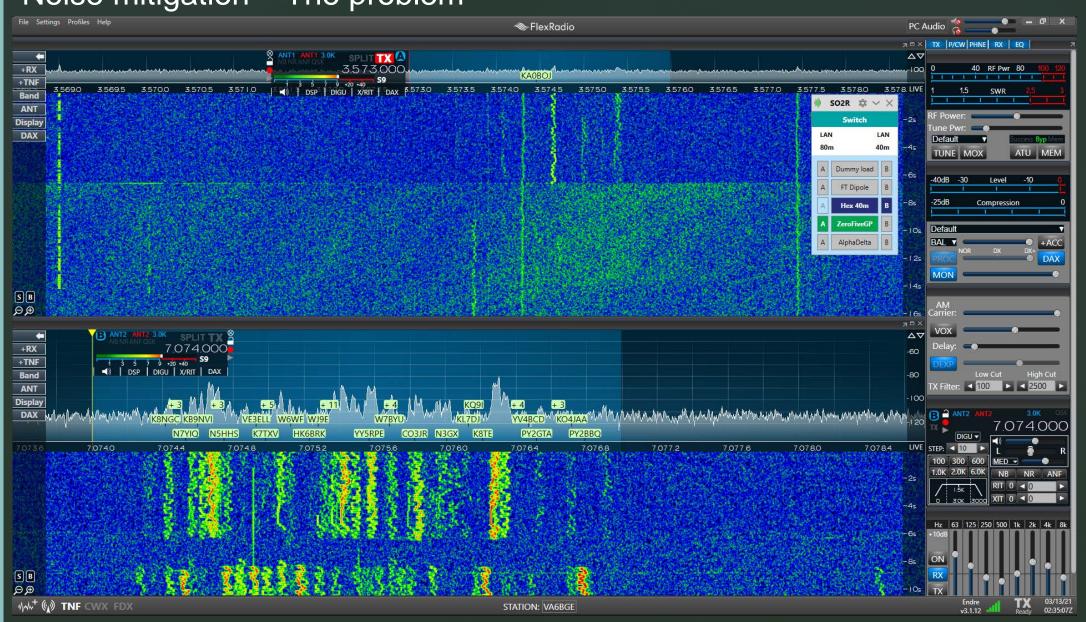


Noise mitigation – The solution

Go for ferrite core transformer – the old way is the quieter way!





Noise mitigation – The result

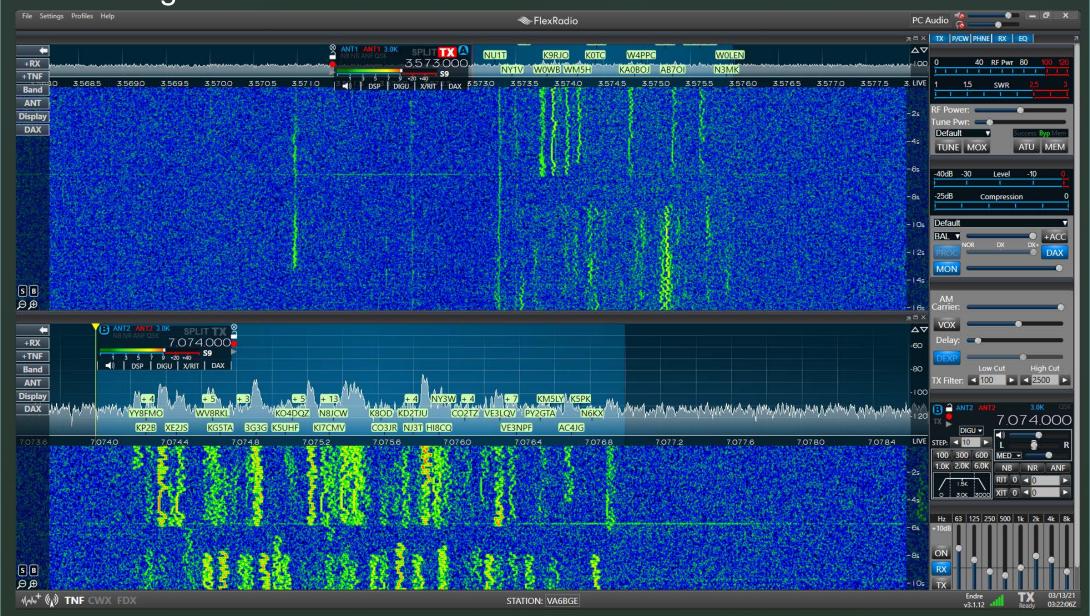


Noise mitigation – Further actions

- Eliminating switching power supplies from the household e.g. cheap phone chargers, have a central charging location at least not to leave them plugged in when not in use,
- Always check on the waterfall if a new device is causing any further noise and take corrective
 actions as necessary or return the product,
- The chokes on the coax cables also helped to reduce some noise,
- Some noise cannot be cut, but therefore there are some smart tools to reduce them.

Noise mitigation – Further actions

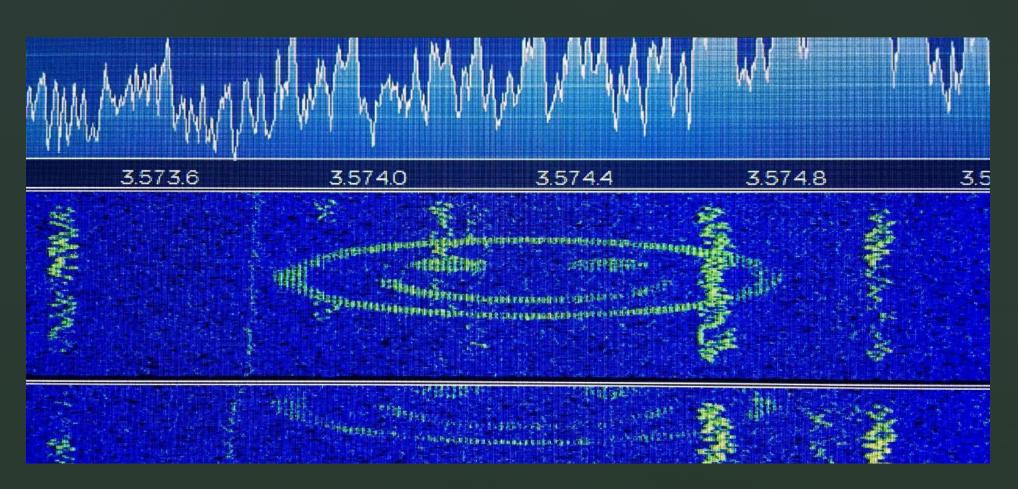Sometime the noise is intentional indeed...



• Contact: Endre Balogh, VA6BGE, balosoft@gmail.com



